

I just wanted to add this to the LED knowledge base 😊

You can easily use the LM317 to regulate current to 3 LEDs (rather than 4)... here's how:


1. Pick out your LEDs (I'm using Red, rated at 20mA max, each).


Note: get some bright ones (mine were 3000MCD I believe) b/c you can always dim them

2. Determine the value of resistance needed: $R=1.2/I$ (where $I=60\text{mA}$ in my case... i.e. $20\text{mA} * 3 = 60\text{mA}$)
So, $R=20$ ohms. And $C=0.1$ microF (though this really isn't needed, it's for filtering noise)

3. Go buy your stuff (LM317 IC, Resistor(s), and LEDs, etc).

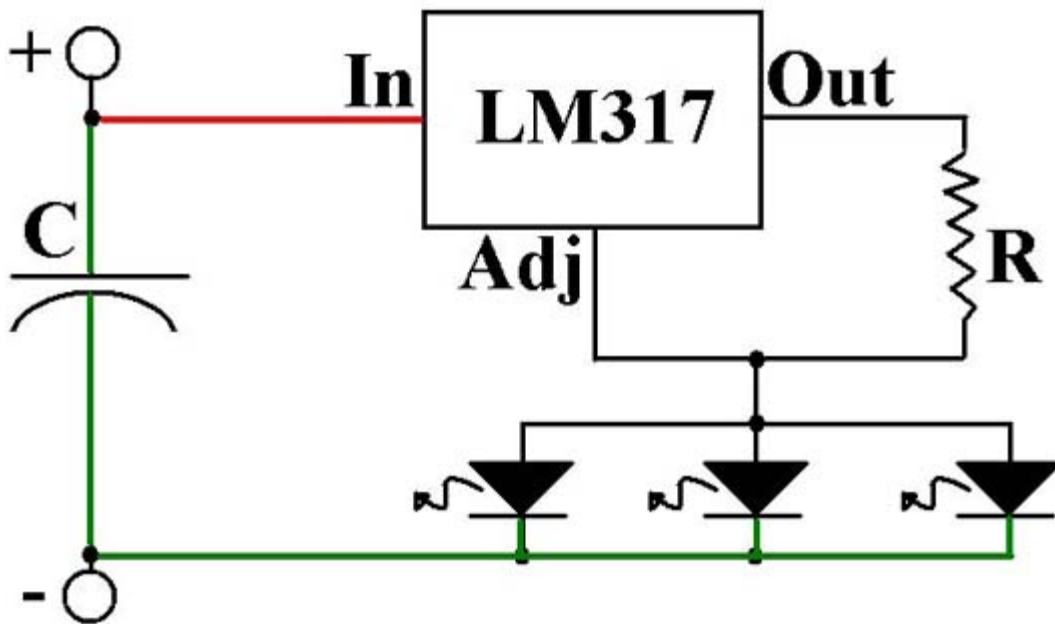4. Wire/solder everything up per the diagram(s)... I did it all as one unit that can easily be installed onto the dash:



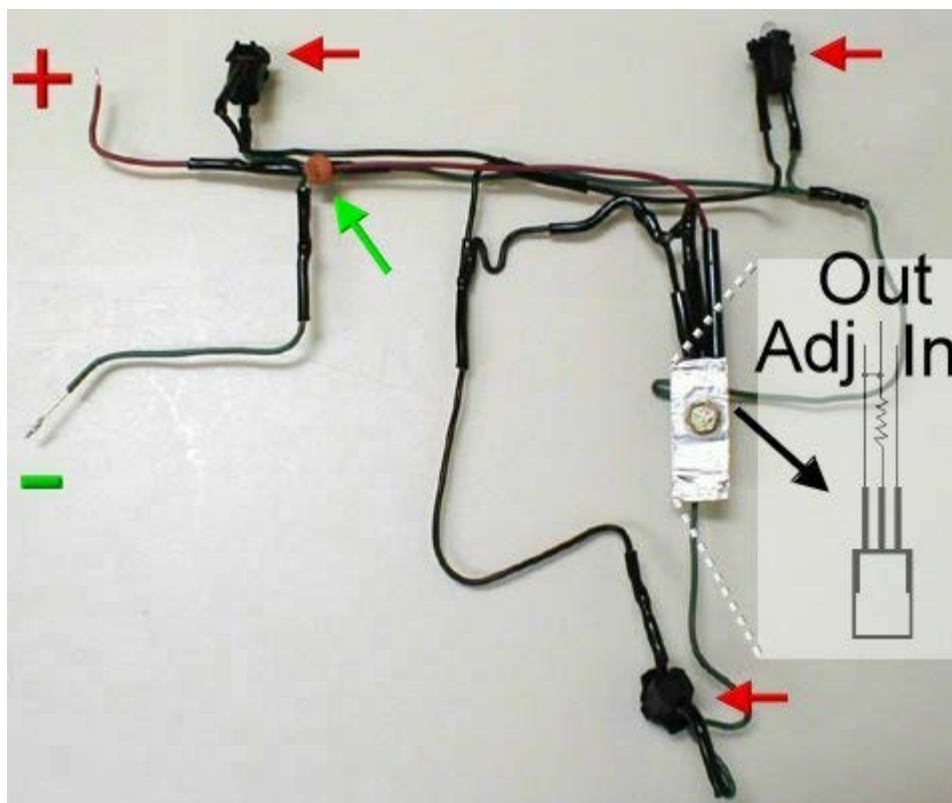

(red arrows are the LEDs, green is capacitor, +/- bias indicated, and the inset shows the connections to the regulator)

5. Test it out before installing (I used the AC/DC converter plugged into my answering machine:



Yep, it works.

Also: I took some sandpaper to the LEDs to roughen them up so they diffuse light better:



(BTW, the pick of lighted LEDs doesn't look very red b/c I too have a cheap digicam)

Anyways... just thought some may want the 3 LEDs rather than 4 (I was just too lazy to drill the 4th hole 😊)